

EC 2254 - LINEAR INTEGRATED CIRCUITS

Time: Three hours

Maximum: 100 Marks

Answer ALL questions

PART A - (10 x 2 = 20 Marks)

1. Define slew rate and CMRR.
2. Why are active loads preferred than passive loads in the input stage of an operational amplifier?
3. Compare the performance of inverting and non inverting operational amplifier configurations.
4. Why is frequency compensation required in operational amplifier?
5. Draw and write equation of an integrator using an op-amp.
6. What is lock range and capture range of PLL?
7. Compare and contrast binary ladder and R-2R ladder DAC?
8. Define resolution and conversion time of DAC.
9. Sketch the monostable multivibrator circuit diagram using IC555.
10. What is meant by thermal shutdown applied to voltage regulators?

PART B - (5 x 16 = 80 Marks)

11. (a) (i) Explain the term epitaxy and describe the epitaxial growth process.
(ii) Describe in detail the processing steps involved in the fabrication of monolithic IC.

Or

- (b) Draw the circuit diagram of the output stage of the IC 741 OP AMP and explain its operation with clearly indicating the protection mechanisms indicated.

12. (a) With relevant circuits, explain the following applications of OPAMP

(i) Voltage to current converters

(ii) Multiplier

Or

(b) (i) Explain the steps involved in the design of a band pass filter using OPAMP.

(ii) Write a note on Schmitt trigger.

13. (a) Draw the functional block schematic of a NE565 PLL and explain the roles of the low pass filter and VCO. Derive the expression for the capture range and lock in range of the PLL.

Or

(b) With suitable block diagram, explain the operation of 566 voltage controlled oscillator. Also derive an expression for the frequency of the output waveform generated.

14. (a) Describe the operation of dual slope and successive approximation type ADC. What are the advantages of dual slope ADC?

Or

(b) (i) Explain voltage mode and current mode operations of R-2R ladder type DAC.

(ii) Discuss the operation of sample and hold circuit with circuit diagram.

15. (a) (i) How can the current drive capability be increased while using three terminal voltage regulators?

(ii) Design an adjustable voltage regulator circuit using LM317 for the following specifications:

Input dc voltage = 13.5 V

Output DC voltage = 5 to 9 V

Load current (maximum) = 1 A

Or

(b) Describe the working of IC723 voltage regulator and explain the importance of current limiting techniques.